

# Basic Computer Architecture

- ▶ Computers consist of:

- ▶ Datapath

- ▶ Control unit

- ▶ It is designed to implement a particular instruction set.

- ▶ The individual instructions are the engineering equivalent of the mathematician's

- ▶  $z=f(x,y)$



# Opcode – Destination -Operands

## ▶ OPCODE

▶ Selects the function

## ▶ DESTINATION

▶ Is nearly always a datapath register

## ▶ OPERANDS

▶ Usually come from datapath register


# Instruction Format Examples

## Register




<https://powcoder.com>

## Immediate

 

## Jump and Branch

 

# Instruction Formats

- ▶ Where DR, SA, SB point to processor registers in the datapath
- ▶ But Operand is itself an immediate operand



# Data and Instructions in Memory

Example for a 16 Bit processor, with 7, 3, 3, 3 bits

Decimal address	Memory contents	Decimal opcode	Other specified fields	Operation
25	0000101 001 010 011	5 (Subtract)	DR:1, SA:2 SB:3	$R1 \leftarrow R2 - R3$
35	0100000 000 100 101	32 (Store)	SA:4 SB:5	$M[R4] \leftarrow R5$
45	1000010 010 111 011	66 (Add Immediate)	DR:2 SA:7 OP:3	$R2 \leftarrow R7 + 3$
55	1100011 101 110 100	96 (Branch on zero)	AD: 44 SA:6	If $R6 = 0$ , $PC \leftarrow PC - 20$
70	0000000 011 000 000	Data = 192. After execution of instruction in 35, Data = 80.		

# User View of Storage

Register  
File  
32 x 32

Program Counter (PC)

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Instruction  
Memory  
 $2^{32} \times 16$

Data  
Memory  
 $2^{32} \times 16$

# Memory Module [entity]

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
entity memory is
    Port ( address : in unsigned std_logic_vector(31 downto 0);
          write_data : in std_logic_vector(31 downto 0);
          MemWrite, MemRead : in std_logic;
          read_data : out std_logic_vector(31 downto 0));
end memory;
```

# Memory Module [architecture]

architecture Behavioral of memory is

-- we will use the least significant 9 bit of the address - array(0 to 512)

type mem\_array is array(0 to 7) of std\_logic\_vector(31 downto 0);

-- define type, for memory arrays

begin

mem\_process: process (address, write\_data)

-- initialize data memory. X denotes hexadecimal number

variable data\_mem : mem\_array := (  
X"00000000", X"00000000", X"00000000", X"00000000",  
X"00000000", X"00000000", X"00000000", X"00000000");

variable addr:integer

begin -- the following type conversion function is in std\_logic\_arith

addr:=conv\_integer(address(2 downto 0));

if MemWrite='1' then

data\_mem(addr):= write\_data;

elsif MemRead='1' then

read\_data <= data\_mem(addr) after 10 ns;

end if;

end process;


end Behavioral;



# A Single-cycle Hardwired Control Unit

- ▶ We briefly consider a system with the simplest possible control unit.
- ▶ The control unit:
  - ▶ Maps each OPCODE to a single datapath operation.
- ▶ Instructions are fetched from an instruction memory
- ▶ This is what all present systems with separate instruction and data code do.

# Single-Cycle Computer

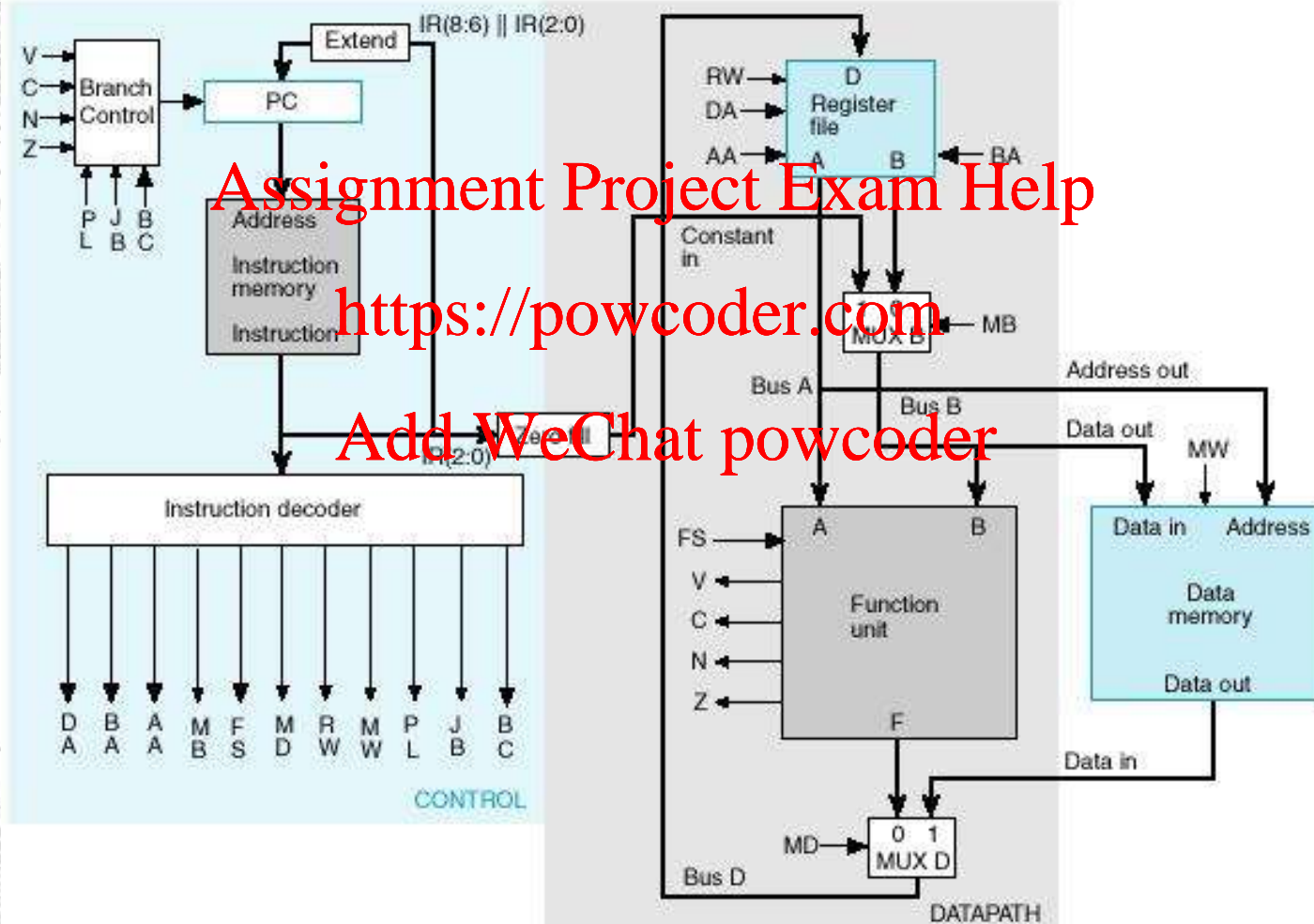

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# Branch

## ► Instruction Bit13=1

► Jump occurs

## ► Instruction Bit13=0

► Conditional Branch occurs

► Bit11, Bit10 and Bit9

► Select the status bit

BC      Status Bit

000

C

001

N

010

V

011

Z

100

C

101

N

110

V

111

Z

# Jump and Branch

► PL=1

► Jump or Branch loading the PC

► PL=0

<https://powcoder.com>

► PC is incremented

Add WeChat powcoder

►  $PL=1 \wedge JB=0$

► Jump

►  $PL=1 \wedge JB=1$

► Conditional branch



# Truth Table BIT15 – BIT13

► The following operations classification helps with the implementation of the instruction decoder

<https://powcoder.com>


Instruction Function Type	Instruction Bits			Control Word Bits					
	Bit 15	Bit 14	Bit 13	MB	MD	RW	MW	PL	JB
ALU function using registers	0	0	0	0	0	1	0	0	X
Shifter function using registers	0	0	1	0	0	1	0	0	X
Memory write using register data	0	1	0	0	X	0	1	0	X
Memory read using register data	0	1	1	0	1	1	0	0	X
ALU operation using a constant	1	0	0	1	0	1	0	0	X
Shifter function using a constant	1	0	1	1	0	1	0	0	X
Conditional Branch	1	1	0	X	X	0	0	1	0
Unconditional Jump	1	1	1	X	X	0	0	1	1

# Instruction Decoder

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

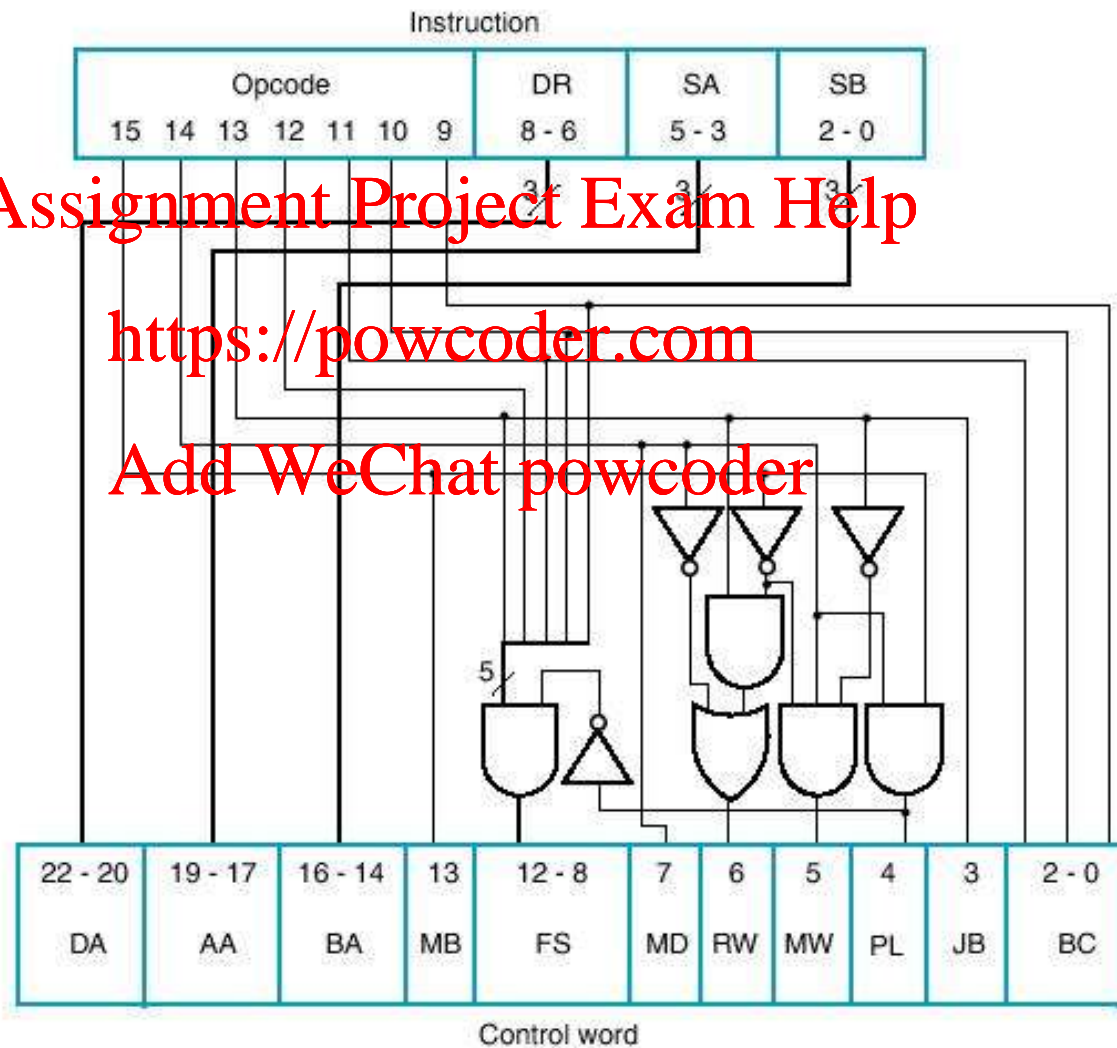

# Single-Cycle Computer Instruction Example

Operation code	Symbolic name	Format	Description	Function	MB	MD	RW	MW	PL	JB
1000010	ADI	Immediate	Add immediate operand	$R[DR] \leftarrow R[SA] + I(1:0)$	1	0	1	0	0	0
0110000	LD	Register	Load memory content into register	$R[DR] \leftarrow M[R[SA]]$	0	1	1	0	0	1
0100000	ST	Register	Store register content in memory	$M[R[SA]] \leftarrow R[SB]$	0	1	0	1	0	0
0011000	SL	Register	Shift left	$R[DR] \leftarrow s!R[SB]$	0	0	1	0	0	1
0001110	NOT	Register	Complement register	$R[DR] \leftarrow \overline{R[SA]}$	0	0	1	0	0	0
1100000	BRZ	Jump/Branch	If $R[SA] = 0$ , branch to $PC + seAD$	If $R[SA] = 0, PC \leftarrow PC + seAD$ , If $R[SA] \neq 0, PC \leftarrow PC + 1$	1	0	0	0	1	0



# Single-cycle Problem

- ▶ A single-cycle control unit cannot implement:
  - ▶ more complex addressing modes
  - ▶ Composite functions
    - ▶ E.g. Multiplication
- ▶ A single-cycle control unit has long worst case delay path.
- ▶ Slow clock.




# Worst Case Delay


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

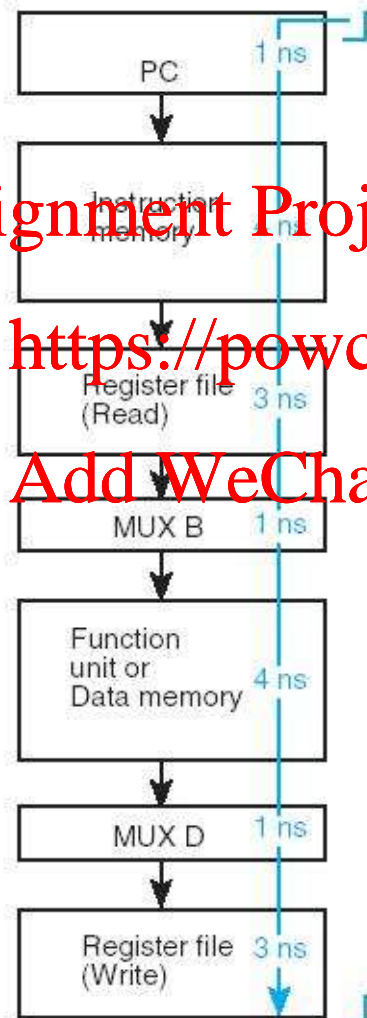
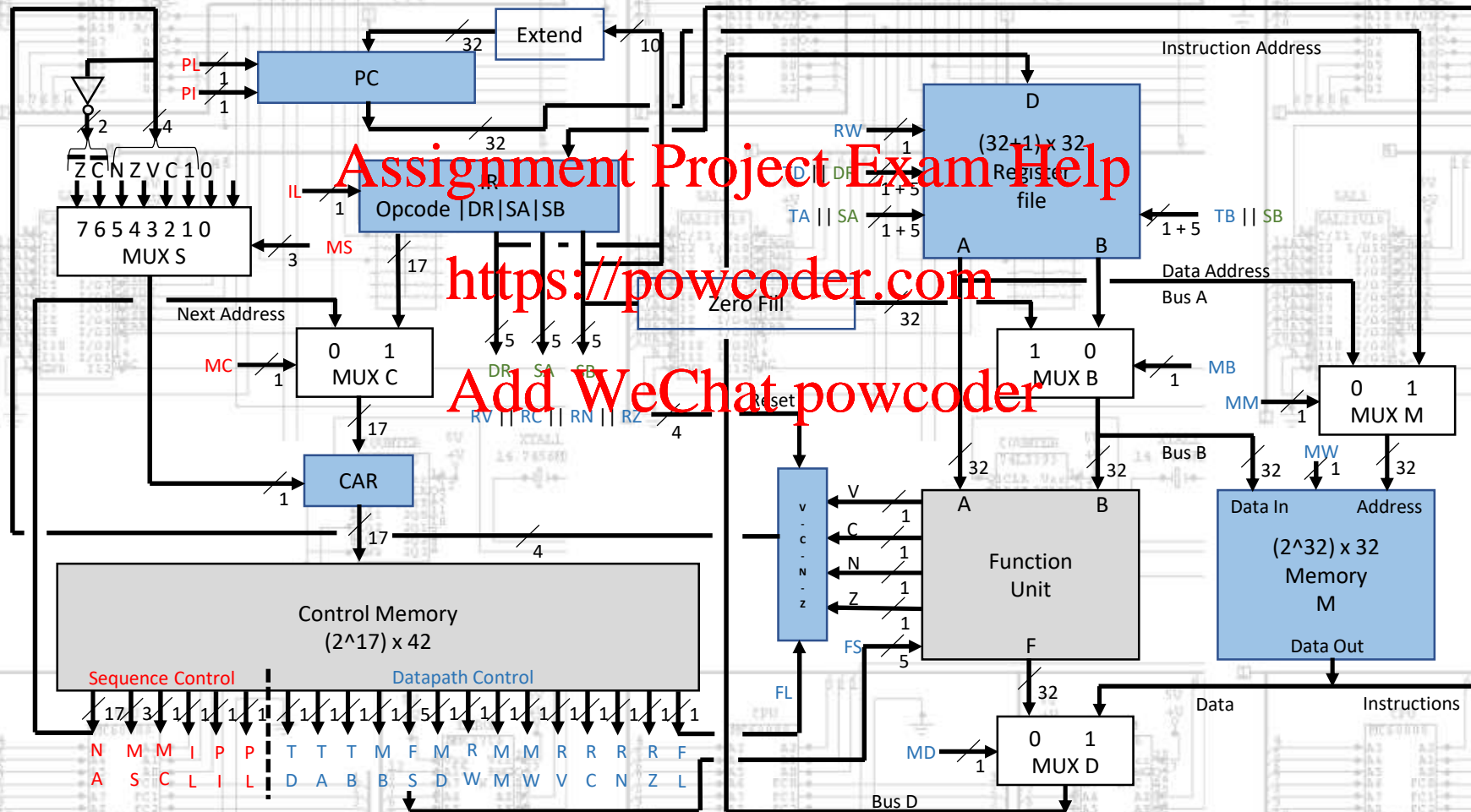
# Multiple-Cycle Microprogrammed Computer




# Microinstruction Format

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

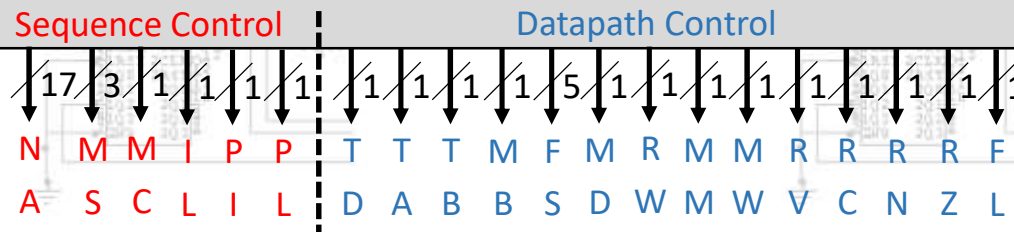

# Control Word Information for Datapath

Example, our project is different!

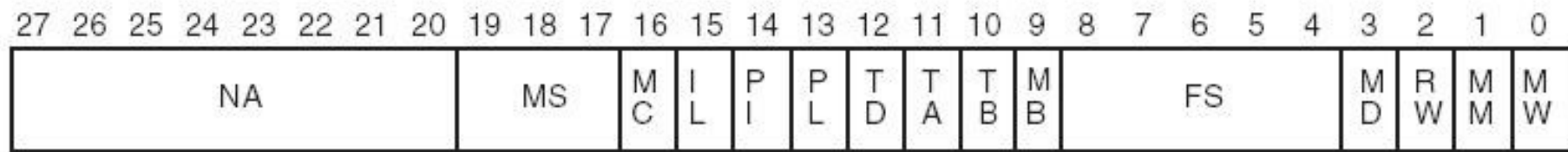

Assignment Project Exam Help

<https://powecoder.com>

Add WeChat powecoder

Assignment Project Exam Help

TD	TA	TB	MB	FS		MD	RW	MM	MW		
Select	Select	Select	Select	Code	Function	Code	Select	Function	Code		
R[DR]	R[SA]	R[SB]	Register	0	$F = A$	00000	FnUt	No write (NW)	Address	No write (NW)	0
R8	R8	R8	Constant	1	$F = A + 1$	00001	PC	Write (WR)	PC	Write (WR)	1
					$F = A + B$	00010					
					$F = A + B + 1$	00011					
					$F = A + \overline{B}$	00100					
					$F = A + \overline{B} + 1$	00101					
					$F = A - 1$	00110					
					$F = A$	00111					
					$F = A \wedge B$	01000					
					$F = A \vee B$	01010					
					$F = A \oplus B$	01100					
					$F = \overline{A}$	01110					
					$F = B$	10000					
					$F = sr\ B$	10100					
					$F = sl\ B$	11000					