

Register File

Top-level Schematic (2 to 4 decoder)

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

Assignment Project Exam Help

```
entity decoder_2to4 is
```

```
Port ( A0 : in std_logic;
```

<https://powcoder.com>

```
    Q0 : out std_logic;
```

```
    Q1 : out std_logic;
```

Add WeChat powcoder

```
    Q2 : out std_logic;
```

```
    Q3 : out std_logic);
```

```
end decoder_2to4;
```

```
architecture Behavioral of decoder_2to4 is
```

```
begin
```

```
Q0<= ((not A0) and (not A1)) after 5 ns;
```

```
Q1<= (A0 and (not A1)) after 5 ns;
```

```
Q2<= ((not A0) and A1) after 5 ns;
```

```
Q3<= (A0 and A1) after 5 ns;
```

```
end Behavioral;
```

Register File

Top-level Schematic (2 to 1 MUX)

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

Assignment Project Exam Help

entity mux2_4bit is
port (In0 : in std_logic_vector(3 downto 0);
In1 : in std_logic_vector(3 downto 0);
S : in std_logic;
Z : out std_logic_vector(3 downto 0));
end mux2_4bit;

architecture Behavioral of mux2_4bit is
begin
Z <= In0 after 5 ns when S='0' else
In1 after 5 ns when S='1' else
"0000" after 5 ns;
end Behavioral;

Register File

Top-level Schematic (4 to 1 MUX)

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux4_4bit is
Port (In0, In1, In2, In3 : in std_logic_vector(3 downto 0);
S0, S1 : in std_logic;
Z : out std_logic_vector(3 downto 0));
end mux4_4bit;

architecture Behavioral of mux4_4bit is
begin
Z <= In0 after 5 ns when S0='0' and S1='0' else
In1 after 5 ns when S0='1' and S1='0' else
In2 after 5 ns when S0='0' and S1='1' else
In3 after 5 ns when S0='1' and S1='1' else
"0000" after 5 ns;
end Behavioral;

Register File

Top-level Schematic (4 to 1 MUX)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity reg4 is
port ( D : in std_logic_vector(3 downto 0);
      Clk : in std_logic;
      Q : out std_logic_vector(3 downto 0));
end reg4;
```


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

```
architecture Behavioral of reg4 is
begin
process(Clk)
begin
if (rising_edge(Clk)) then
if load='1' then
Q<=D after 5 ns;
end if;
end if;
end process;
end Behavioral;
```

Register File Top-level Schematic

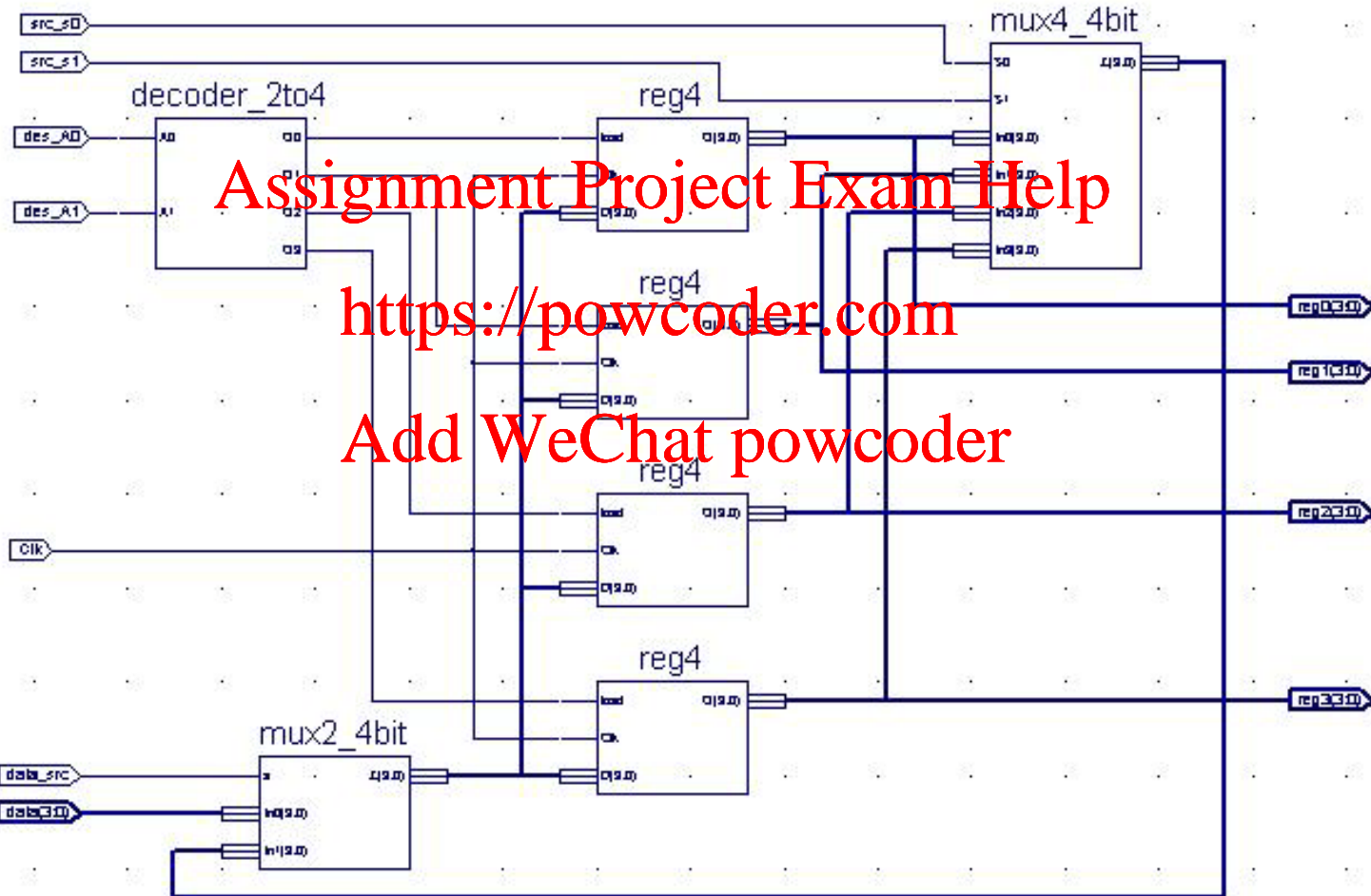

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Register File

Top-level VHDL (`entity register_file`)

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

Assignment Project Exam Help

`entity register_file is`
`Port (src_s0 : in std_logic;`
<https://powcoder.com>

Add WeChat powcoder

```
src_s1 : in std_logic;  
des_A0 : in std_logic;  
des_A1 : in std_logic;  
Clk : in std_logic;  
data_src : in std_logic;  
data : in std_logic_vector(3 downto 0);  
reg0 : out std_logic_vector(3 downto 0);  
reg1 : out std_logic_vector(3 downto 0);  
reg2 : out std_logic_vector(3 downto 0);  
reg3 : out std_logic_vector(3 downto 0);  
end register_file;
```

Register File

Top-level VHDL (**COMPONENT** reg4)

architecture Behavioral of register_file is

-- components
Assignment Project Exam Help

-- 4 bit Register for register file
<https://powcoder.com>

COMPONENT reg4
PORT(
 DATA : **IN** **std_logic_vector**(3 **downto** 0);
 load : **IN** **std_logic**;
 Clk : **IN** **std_logic**;
 Q : **OUT** **std_logic_vector**(3 **downto** 0)
);

END COMPONENT;

Register File

Top-level VHDL (**COMPONENT** decoder_2to4/ mux2_4bit)

-- 2 to 4 Decoder

COMPONENT decoder_2to4

PORT(

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

A0 : IN std_logic;
A1 : IN std_logic;
Q0 : OUT std_logic;
Q1 : OUT std_logic;
Q2 : OUT std_logic;
Q3 : OUT std_logic;

END COMPONENT;

-- 2 to 1 line multiplexer

COMPONENT mux2_4bit

PORT(

In0 : IN std_logic_vector(3 downto 0);
In1 : IN std_logic_vector(3 downto 0);
s : IN std_logic;
Z : OUT std_logic_vector(3 downto 0);

END COMPONENT;

Register File

Top-level VHDL (**COMPONENT** decoder_2to4/ mux2_4bit)

-- 2 to 4 Decoder

```
COMPONENT decoder_2to4  
PORT(
```

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

```
A0 : IN std_logic;  
A1 : IN std_logic;  
Q0 : OUT std_logic;  
Q1 : OUT std_logic;  
Q2 : OUT std_logic;  
Q3 : OUT std_logic;  
);
```

```
END COMPONENT;
```

-- 2 to 1 line multiplexer

```
COMPONENT mux2_4bit  
PORT(
```

```
In0 : IN std_logic_vector(3 downto 0);  
In1 : IN std_logic_vector(3 downto 0);  
s : IN std_logic;  
Z : OUT std_logic_vector(3 downto 0)  
);
```

```
END COMPONENT;
```

Register File

Top-level VHDL (**COMPONENT** mux4_4bit)

-- 4 to 1 line multiplexer

COMPONENT mux4_4bit

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

In0 : **IN** std_logic_vector(3 downto 0);

In1 : **IN** std_logic_vector(3 downto 0);

In2 : **IN** std_logic_vector(3 downto 0);

In3 : **IN** std_logic_vector(3 downto 0);

S0 : **IN** std_logic;

S1 : **IN** std_logic;

Z : **OUT** std_logic_vector(3 downto 0)

);

END COMPONENT;

-- signals

signal load_reg0, load_reg1, load_reg2, load_reg3 : std_logic;

signal reg0_q, reg1_q, reg2_q, reg3_q,

data_src_mux_out, src_reg : std_logic_vector(3 downto 0);

Register File

Top-level VHDL (port maps 1)

begin

-- port maps ;)

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

reg00: reg4 PORT MAP(
D => data_src_mux_out,
load => load_reg0,
Clk => Clk,
Q => reg0_q
);

-- register 1

reg01: reg4 PORT MAP(
D => data_src_mux_out,
load => load_reg1,
Clk => Clk,
Q => reg1_q
);

CS2022

Register File

Top-level VHDL (port maps 2)

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

```
-- register 2
reg02: reg4 PORT MAP(
    D => data_src_mux_out,
    load => load_reg2,
    Clk => Clk,
    Q => reg2_q
);

-- register 3
reg03: reg4 PORT MAP(
    D => data_src_mux_out,
    load => load_reg3,
    Clk => Clk,
    Q => reg3_q
);

-- Destination register decoder
des_decoder_2to4: decoder_2to4 PORT MAP(
    A0 => des_A0,
    A1 => des_A1,
    Q0 => load_reg0,
    Q1 => load_reg1,
    Q2 => load_reg2,
    Q3 => load_reg3
);
```

Register File

Top-level VHDL (port maps 3)

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

```
-- 2 to 1 Data source multiplexer
data_src_mux2_4bit: mux2_4bit PORT MAP(
    In0 => data,
    In1 => src_reg,
    S => data_src,
    Z => data_src_mux_out
);

-- 4 to 1 source register multiplexer
Inst_mux4_4bit: mux4_4bit PORT MAP(
    In0 => reg0_q,
    In1 => reg1_q,
    In2 => reg2_q,
    In3 => reg3_q,
    S0 => src_s0,
    S1 => src_s1,
    Z => src_reg
);

reg0 <= reg0_q;
reg1 <= reg1_q;
reg2 <= reg2_q;
reg3 <= reg3_q;
end Behavioral;
```

Register File

Top-level VHDL (Schematic)

register_file

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

```
src_s0 reg0(3:0)
src_s1
des_A0 reg1(3:0)
des_A1
Clk reg2(3:0)
data_src reg3(3:0)
data(3:0)
```