

# Concurrent **S**ignal **A**ssignment Statements (**CSAs**)

- ▶ Digital systems operate with concurrent signals
- ▶ Signals are assigned values at a specific point in time. **Assignment Project Exam Help**  
<https://powcoder.com>
- ▶ VHDL uses **signal assignment** statements
  - ▶ Specify value and time
- ▶ Multiple **signal assignment** statements are executed concurrently
- ▶ Concurrent **S**ignal **A**ssignment Statements (**CSAs**)

# Half-Adder CSA

► VHDL must specify:

► Events **Assignment Project Exam Help**

► Delays **<https://powcoder.com>**

► Concurrency

**Add WeChat powcoder**

**architecture** concurrent\_behavior **of** half\_adder **is**  
**begin**

sum <= (x **xor** y) **after** 5 ns;

carry <= (x **and** y) **after** 5 ns;


**end** concurrent\_behavior;

# CSA Statements

- ▶ concurrent\_behavior
- ▶ Name of architecture that defines the half\_adder entity.
- ▶ signal assignment statements
  - ▶ `sum <= (x xor y) after 5 ns;`
  - ▶ `carry <= (x and y) after 5 ns;`
- ▶ Signal assignment operator `<=`
  - ▶ Describes how output signals depend on input signals
  - ▶ An output signal changes if an input signal has changed.

# Half Adder Operation

Event

 

# after Keyword

- ▶ Signal propagation of the XOR and AND gates must be taken into account.
- ▶ Both gates require 5 ns propagation delay
- ▶ **signal assignment** statements define this through the **after** Keyword.
- ▶ This keyword specifies when the output signal is set to the result of an evaluation after an input signal transition (event).
- ▶ The textual order of the assignment statement has no influence on the timing.

# library and use clauses

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

Assignment Project Exam Help  
entity 2BA4 is

... <https://powcoder.com>

Add WeChat powcoder

- ▶ A library contains design entities that be used
- ▶ The **library** IEEE clause defines the IEEE library.
- ▶ The library may contain packages.
- ▶ The above example specifies through the **use** clause the IEEE.STD\_LOGIC\_1164.**ALL** packages.
- ▶ This package is required for **std\_logic** type declaration.

# Full-Adder VHDL

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

Assignment Project Exam Help


```
entity full_adder is  
    Port (in1, in2, c_in: in std_ulogic;  
          sum, c_out: out std_ulogic );  
end full_adder;
```

<https://powcoder.com>

```
architecture dataflow of full_adder is  
    signal s1,s2,s3: std_ulogic;  
    constant gate_delay: Time := 5 ns;
```

```
begin  
    s1 <= (In1 xor In2) after gate_delay;  
    s2 <= (c_in and s1) after gate_delay;  
    s3 <= (In1 and In2) after gate_delay;  
    sum <= (s1 xor c_in) after gate_delay;  
    c_out <= (s2 or s3) after gate_delay;  
end dataflow;
```

# Full-Adder Schematic

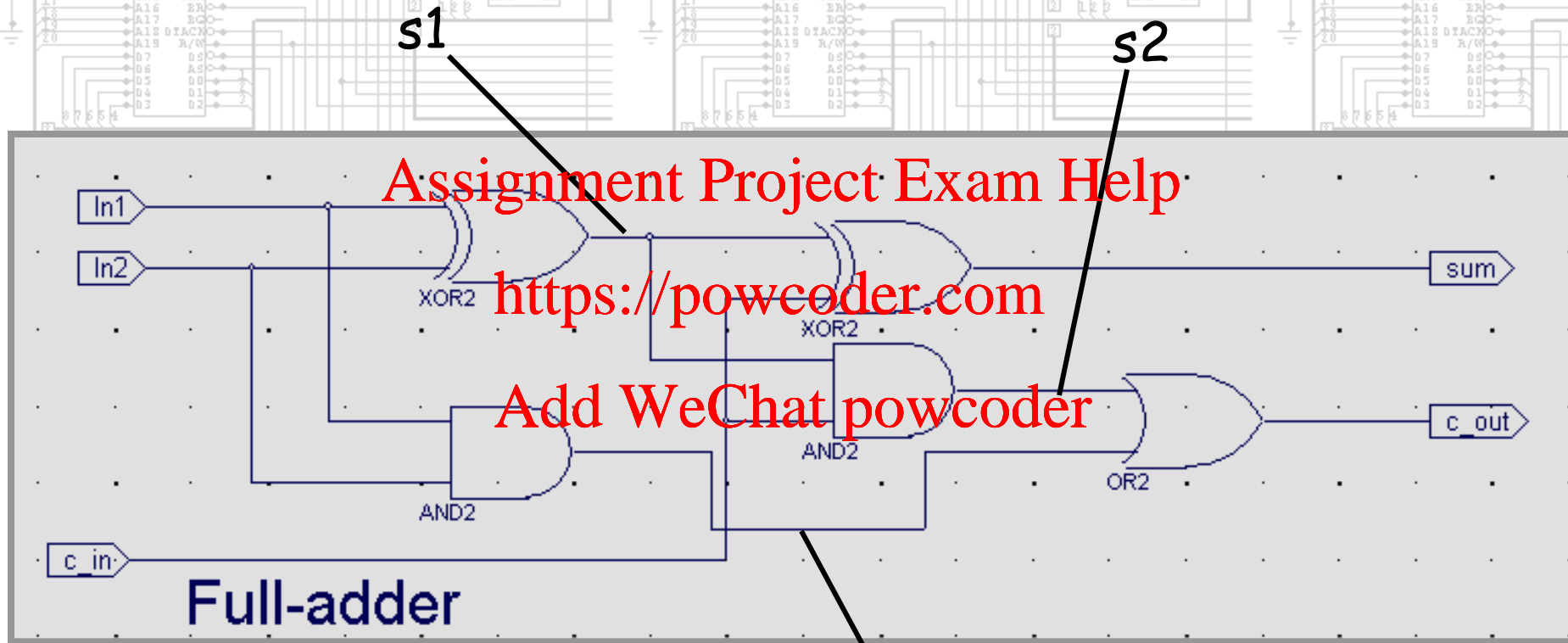

s3



# Architecture Declaration

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

## Assignment Project Exam Help

```
Port (in1, in2, c_in:in std_ulogic;  
      sum, c_out:out std_ulogic );  
end full_adder;
```

```
architecture dataflow of full_adder is  
  signal s1,s2,s3: std_ulogic;
```

```
  constant gate_delay: Time := 5ns;
```

```
  begin
```

```
    s1 <= (In1 xor In2) after gate_delay;
```

```
    s2 <= (c_in and s1) after gate_delay;
```

```
    s3 <= (In1 and In2) after gate_delay;
```

```
    sum <= (s1 xor c_in) after gate_delay;
```

```
    c_out <= (s2 or s3) after gate_delay;
```

```
  end dataflow;
```

# Architecture Body

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

## Assignment Project Exam Help

```
Port (in1, in2, c_in:in std_ulogic;  
      sum, c_out:out std_ulogic );  
end full_adder;
```

```
architecture dataflow of full_adder is  
  signal s1,s2,s3: std_ulogic;  
  constant gate_delay: Time := 5ns;  
begin
```

```
  s1 <= (In1 xor In2) after gate_delay;  
  s2 <= (c_in and s1) after gate_delay;  
  s3 <= (In1 and In2) after gate_delay;  
  sum <= (s1 xor c_in) after gate_delay;  
  c_out <= (s2 or s3) after gate_delay;  
end dataflow;
```

# The Full-Adder Model

- ▶ The full-adder simulates the signal transitions at gate-level
- ▶ The model has three internal signals
- ▶ These signals are not ports to the entity
- ▶ The internal signals are declared in the architectural declaration
- ▶ The Boolean equations define how each signal is derived as function of:
  - ▶ Other signals
  - ▶ Propagation delay
- ▶ **Constant** can be used to declare a constant of a particular type.

In this case **Time**

# Signals

► Signals are not variables

► History of values over time

► Waveform

Assignment Project Exam Help

```
signal s1: std_ulogic := '0';
```

<https://powcoder.com>

► Signals may use the assignment symbol := followed by an expression

Add WeChat powcoder

► The value of the expression will be initial value of the signal

► If no initialisation is provided the signal receives a default value

► VHDL signal types:

► Integer, real, bit\_vector...

# Signals and Time

- ▶ A concurrent signal assignment statement (CSA)

```
sum <= (x xor y) after 5 ns;
```

Assignment Project Exam Help

- ▶ In a more general form:

<https://powcoder.com>

- ▶ signal <= value expression after time expression;

- ▶ In the example

Add WeChat powcoder

- ▶ if **x** or **y** change its value the **sum** will be assigned the result of the (x xor y) evaluation after 5ns.
- ▶ The Time-value pair represents the future value of the signal.
- ▶ Also called transaction.

# Multiple Signal Transactions

- It is possible to specify the following:

```
s1 <= (x xor y) after 5 ns, (x or y) after 10 ns, (not x) after 10 ns;
```

- After one of the signals changed all three waveform elements will be evaluated and scheduled according to their after specification.
- The simulation keeps an ordered list of all transactions scheduled for a particular signal.
- The scheduled transactions are also known as:
  - Projected output waveform.


# Waveform Specification

▶ The following CSA will generate the following waveform:

Assignment Project Exam Help

```
s2 <= '0', '1' after 10 ns, '0' after 20 ns, '1' after 40 ns;
```

Add WeChat powcoder

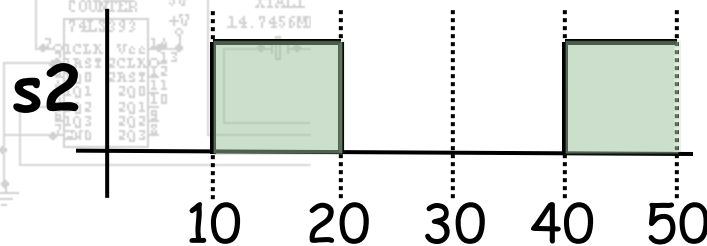

# Resolved Signals

- ▶ In a physical system a wire (signal) has a driver.
- ▶ This driver determines the waveform.
- ▶ Up to now every signal had one driver only
- ▶ But real systems have shared signals:
  - ▶ Buses
  - ▶ Wired logic
- ▶ VHDL determines the value of the signal with multiple drivers through a resolution function.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



# Resolved Type Declaration

- ▶ A shared signal must be declared as a resolved type.
- ▶ The previous examples used unresolved types:

`std_ulogic_vector(7 downto 0);`  
`std_ulogic;`

<https://powcoder.com>  
Add WeChat powcoder

- ▶ The following declaration will make these signal types resolved:

```
std_logic_vector(7 downto 0);  
std_logic;
```