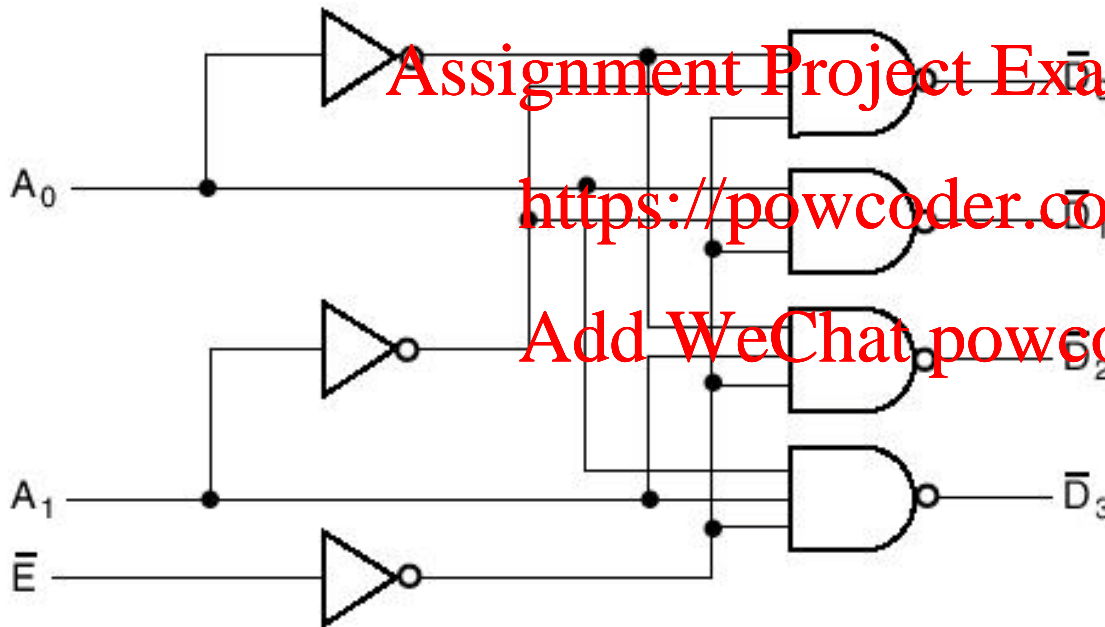


2 to 4 Line Decoder Structural



\bar{E}	A_1	A_0	\bar{D}_0	\bar{D}_1	\bar{D}_2	\bar{D}_3
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

(b) Truth table

$$\bar{D}_0 = \overline{E \bar{A}_1 \bar{A}_0}$$

$$\bar{D}_1 = \overline{E \bar{A}_1 A_0}$$

$$\bar{D}_2 = \overline{E A_1 \bar{A}_0}$$

$$\bar{D}_3 = \overline{E A_1 A_0}$$

2 to 4 Line Decoder (Page 1)

Structural

-- 2-to-4 Line Decoder: Structural VHDL Description

library ieee, lcdf_vhdl;

use ieee.std_logic_1164.all; use lcdf_vhdl.pkg_prims.all;

entity decoder_2_to_4 is

port(E, A0, A1: in std_logic;
D0, D1, D2, D3: out std_logic);

end decoder_2_to_4;

architecture structural_1 of decoder_2_to_4 is

component NOT1

port(in1: in std_logic;
out1: out std_logic);

end component;


2 to 4 Line Decoder (Page 3)

Structural

```
component NAND3
  port(in1, in2, in3: in std_logic;
        out1: out std_logic);
end component;

signal not_A0, not_A1: std_logic;
begin
  g0: NOT1 port map (in1 => A0, out1 => not_A0);
  g1: NOT1 port map (in1 => A1, out1 => not_A1);
  g2: NAND3 port map (in1 => not_A0, in2 => not_A1,
                      in3 => E, out1 => D0);
  g3: NAND3 port map (in1 => A0, in2 => not_A1,
                      in3 => E, out1 => D1);
  g4: NAND3 port map (in1 => not_A0, in2 => A1,
                      in3 => E, out1 => D2);
  g5: NAND3 port map (in1 => A0, in2 => A1,
                      in3 => E, out1 => D3);
end structural_1;
```

4 to 1 Line Multiplexer

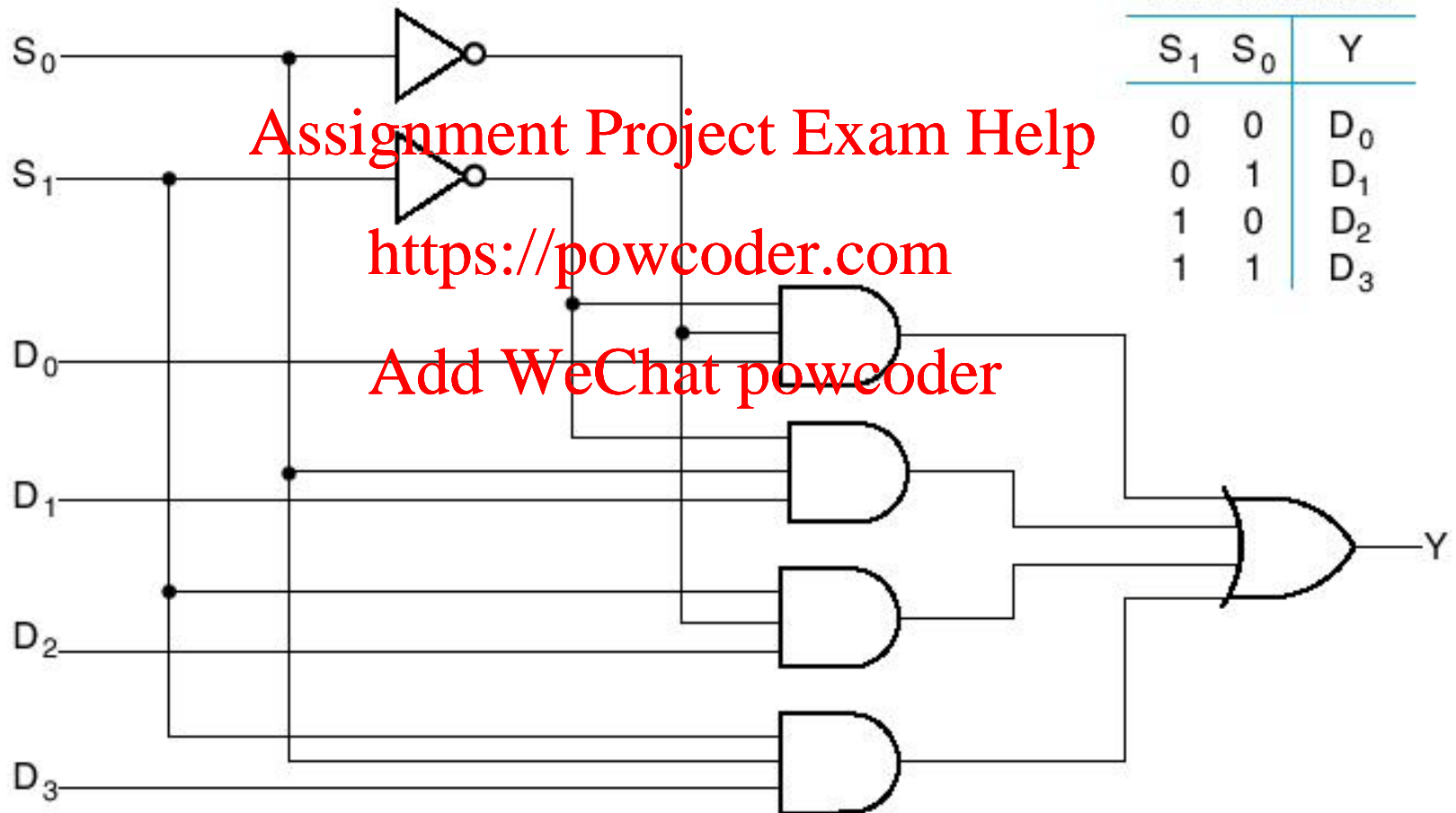

Function table

S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

4 to 1 Line Multiplexer (Page 1)

-- 4-to-1 Line Multiplexer: Structural VHDL Description

```
library ieee, lcdf_vhdl;
```

```
use ieee.std_logic_1164.all, lcdf_vhdl.func_prims.all;
```

```
entity multiplexer_4_to_1 is
```

```
    port(S: in std_logic_vector(0 to 1);
```

```
          D: in std_logic_vector(0 to 3);
```

```
          Y: out std_logic);
```

```
end multiplexer_4_to_1_st;
```

```
architecture structural_2 of multiplexer_4_to_1_st is
    component NOT1
```

```
        port(in1: in std_logic;
```

```
              out1: out std_logic);
```

```
    end component;
```

```
    component AND3
```

```
        port(in1, in2, in3: in std_logic;
```

```
              out1: out std_logic);
```

```
    end component;
```

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

4 to 1 Line Multiplexer (Page 2)


```
component OR4
port(in1, in2, in3, in4: in std_logic;
out1: out std_logic);
end component;
```

```
signal not_S: std_logic_vector(0 to 1);
signal N: std_logic_vector(0 to 3);
begin
g0: NOT1 port map (S(0), not_S(0));
g1: NOT1 port map (S(1), not_S(1));
g2: AND3 port map (not_S(1), not_S(0), D(0), N(0));
g3: AND3 port map (not_S(1), S(0), D(1), N(1));
g4: AND3 port map (S(1), not_S(0), D(2), N(2));
g5: AND3 port map (S(1), S(0), D(3), N(3));
g6: OR4 port map (N(0), N(1), N(2), N(3), Y);
end structural_2;
```

2 to 4 Line Decoder

Dataflow

Same as slide 1

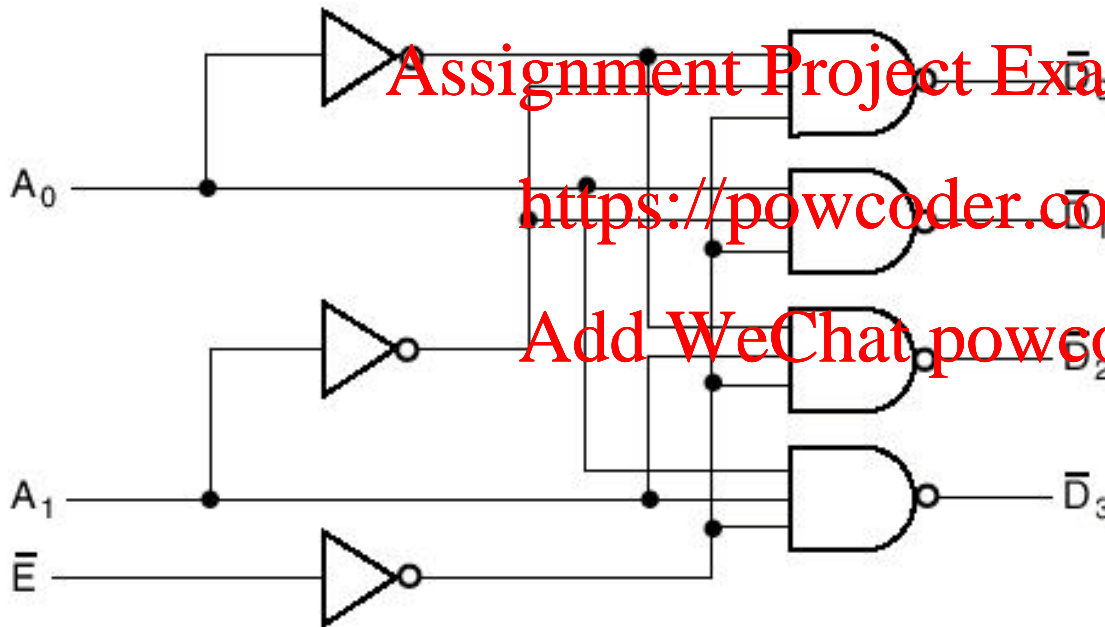

\bar{E}	A_1	A_0	\bar{D}_0	\bar{D}_1	\bar{D}_2	\bar{D}_3
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

(b) Truth table

$$\bar{D}_0 = \overline{E \bar{A}_1 \bar{A}_0}$$

$$\bar{D}_1 = \overline{E \bar{A}_1 A_0}$$

$$\bar{D}_2 = \overline{E A_1 \bar{A}_0}$$

$$\bar{D}_3 = \overline{E A_1 A_0}$$

2 to 4 Line Decoder(Page 1)

Dataflow

-- 2-to-4 Line Decoder: Dataflow VHDL Description

library ieee, lcdf_vhdl;

use ieee.std_logic_1164.all, lcdf_vhdl.func_prims.all;

entity decoder_2_to_4 is

port(E, A0, A1: in std_logic;
D0, D1, D2, D3: out std_logic);

end decoder_2_to_4;

architecture dataflow_1 of decoder_2_to_4 is

signal not_A0, not_A1: std_logic;

begin

not_A0 <= not A0;

not_A1 <= not A1;

D0 <= not (not_A0 and not_A1 and E);

D1 <= not (A0 and not_A1 and E);

D2 <= not (not_A0 and A1 and E);

D3 <= not (A0 and A1 and E);

end dataflow_1;

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

4 to 1 Line Multiplexer

Conditional Dataflow (When-Else)

Same as slide 4

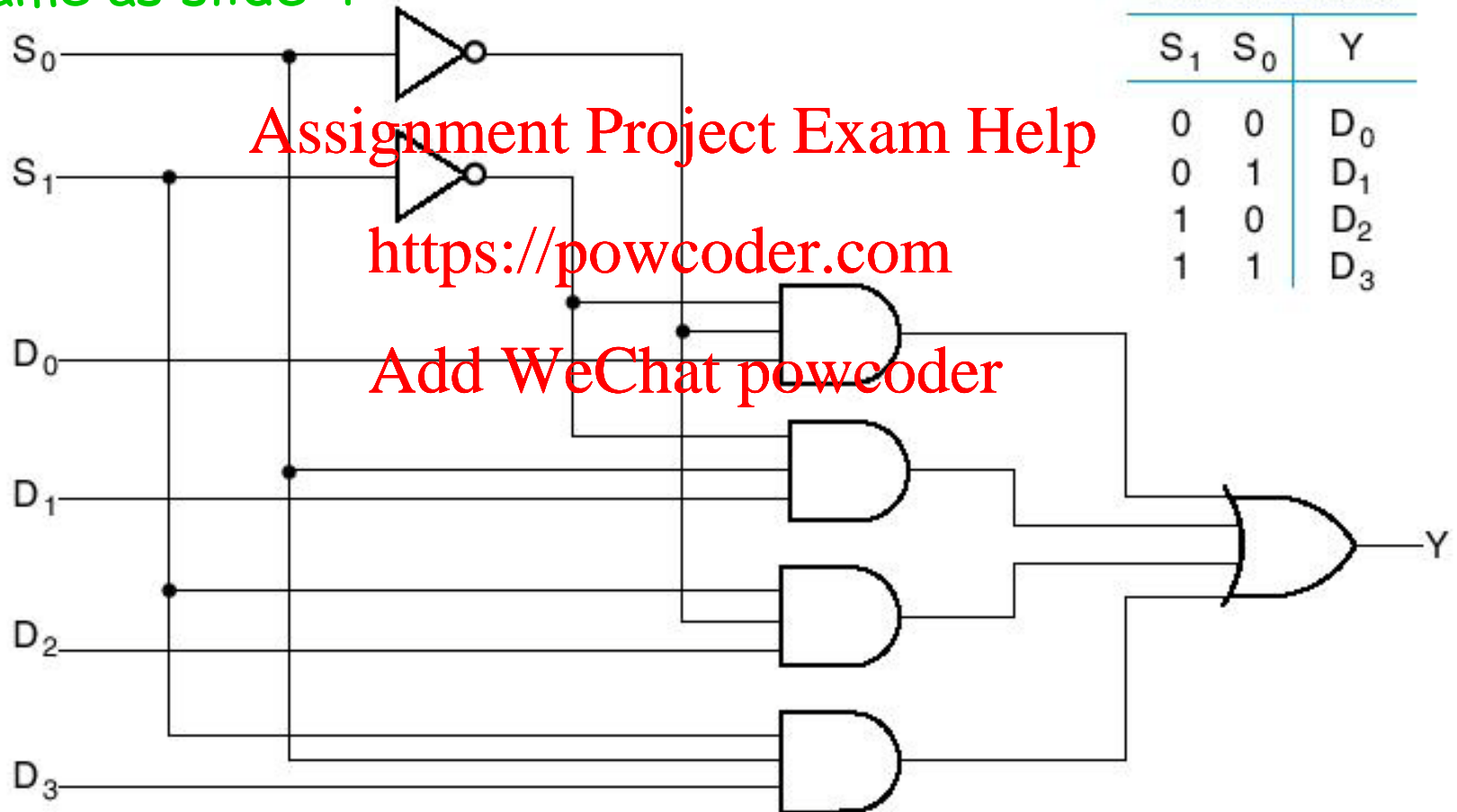

Function table

S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

4 to 1 Line Multiplexer (Page 1)

Conditional Dataflow (When-Else)

```
library ieee;
use ieee.std_logic_1164.all;
entity multiplexer_4_to_1_we is
    port (S : in std_logic_vector(1 downto 0);
          D : in std_logic_vector(3 downto 0);
          Y : out std_logic);
end multiplexer_4_to_1_we;

architecture function_table of multiplexer_4_to_1_we is
begin
    Y <= D(0) when S = "00" else
        D(1) when S = "01" else
        D(2) when S = "10" else
        D(3) when S = "11" else
        'X';
end function_table;
```

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

4 to 1 Line Multiplexer (Page 1)

Conditional Dataflow (With-Select)

```
library ieee;
use ieee.std_logic_1164.all;
entity multiplexer_4_to_1_ws is
    port (S : in std_logic_vector(1 downto 0);
          D : in std_logic_vector(3 downto 0);
          Y : out std_logic);
end multiplexer_4_to_1_ws;

architecture function_table_ws of multiplexer_4_to_1_ws is
begin
    with S select
        Y <= D(0) when "00",
              D(1) when "01",
              D(2) when "10",
              D(3) when "11",
              'X' when others;
end function_table_ws;
```